

DCPH – 401

IV Semester B.Sc. Examination, September/October 2023

(NEP – Freshers)

PHYSICS (Paper – IV)

Thermal Physics and Electronics

Time : 2½ Hours

Max. Marks : 60

Instruction : All Parts are compulsory.

PART – A

I. Answer **any four** questions, **each** carries **two** marks : (4×2=8)

- 1) State first law of thermodynamics.
- 2) Does the efficiency of a Carnot engine depend on the nature of working substance ? Explain.
- 3) What is a perfect black body ? Explain.
- 4) Why the field effect transistor so called ? Explain.
- 5) Op-amp can be used as a voltage multiplier. Explain.
- 6) NAND gate is called a universal gate. Why ?

PART – B

II. Solve **any four** of the following, **each** carries **five** marks : (4×5=20)

- 7) A gas of volume 2m^3 at a pressure of $4 \times 10^5 \text{ N/m}^2$ is compressed adiabatically to a volume of 0.5 m^3 . Calculate the workdone during the process ($\gamma = 1.4$).
- 8) A refrigerator placed in a room at 300 K has inside temperature of 260 K. How many calories of heat shall be delivered to the room for each 1 kcal energy consumed by the refrigerator.
- 9) Calculate the change in melting point of ice when it is subjected to a pressure of 50 atmosphere. Density of ice 917 kg/m^3 , density of water 1000 kg/m^3 and latent heat of ice $336 \times 10^3 \text{ J/kg}$.
- 10) In a half wave rectifier the secondary voltage of the transformer is 30V, if the diode resistance is 25Ω and load resistance is 100Ω . Find the output dc voltage, average value of current and ripple factor.

P.T.O.



- 11) In a non-inverting summing amplifier $R_1 = 1K\Omega$, $R_2 = 2K\Omega$ and $R_3 = 5K\Omega$, if $V_1 = 1V$, $V_2 = 2V$ and $V_3 = 3V$. Calculate input currents and the output voltage if $R_f = 10 K\Omega$.
- 12) Convert the decimal numbers 57 and 75 into their binary equivalent numbers.

PART – C

- III. Answer **any four** questions. **Each** question carries **eight** marks : (4×8=32)
- 13) Obtain an expression for thermal efficiency of a Carnot's engine. 8
- 14) a) State and explain the law of equipartition of energy. 8
 b) Derive an expression for specific heat of gases. (4+4)
- 15) Deduce Planck's law of radiation. 8
- 16) Obtain an expression for carrier concentration in an intrinsic semiconductor. 8
- 17) Explain with a circuit diagram transistor characteristics in common-emitter configuration. 8
- 18) Explain the working of logic gates OR, AND, NOR and NAND, write the corresponding gate symbols and the truth tables. 8

